



বিদ্যাসাগর বিশ্ববিদ্যালয়  
**VIDYASAGAR UNIVERSITY**

**Question Paper**

**B.Sc. Honours Examinations 2020**

(Under CBCS Pattern)

**Semester - III**

**Subject: PHYSICS**

**Paper: C7T & C7P**

**(Digital System and Applications)**

**Full Marks : 60**

**Time : 3 Hours**

*Candidates are required to give their answer in their own words as far as practicable.*

*The figures in the margin indicate full marks.*

**Group - A**

**THEORY (Marks : 40)**

Answer any **two** from the following questions :

2×20

1. Answer any **five** questions from the following :

5×4

(a) State Demorgan's theorem for Boolean algebra.

(b) Write down the drawback of ICs.

(c) Why NAND and NOR gates are called universal gates ?

- (d) Give the idea of RAM and ROM.
- (e) What is race around condition in J-K flip flop ?
- (f) Convert  $(257.5)_8$  into decimal equivalent.
2. (a) (i) Draw the pin diagram of IC-555. 6
- (ii) Add the two number using 2's complement method 0010000 and 11101000. 6
- (b) Draw the circuit diagram of RS flip flop using NOR gate and give the truth table of RS flip flop. 6
- (c) (i) Write down the definition of Register.
- (ii) Classify the register depending on form of entering and retrieving data in a register. 8
3. (a) Design a 4 : 1 multiplexer. 6
- (b) What is counter ? Write down the difference between half adder and full adder. Write the full form of VLSI. What is encoder ? 8
- (c) Draw a circuit diagram of 4 –bit shift register using D – flip flop and explain its operation assuming data word “1011”. 6
4. (a) Implement the Boolean expression  $f(A, B, C) = \sum m(0, 3, 4, 7)$  by Karnaugh map. 6
- (b) Construct AND gate using transistor and explain its operation. 6
- (c) Write the difference between analog and digital circuit. Give the examples of linear and digital ICs. Give truth table of X-OR gate. 8

**Group - B**

**PRACTICAL (Marks : 20)**

Answer any *one* from the following questions :

1×20

1. (a) Verify and design AND, OR and NOT gates using NAND gates..
  - (b) Write down the related theory and truth table only related to these.
  - (c) Draw the circuit diagram for this experiment.
2. (a) Design a switch (NOT gate) using a transistor.
  - (b) Write down the working formula and truth table related to these.
  - (c) Draw the circuit diagram for this experiment.
3. (a) Design an astable multivibrator using 555 timer.
  - (b) Write down the working formula only related to these.
  - (c) Draw the circuit diagram for this experiment.

\_\_\_\_\_